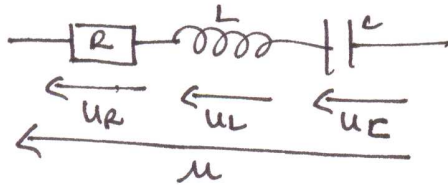


# Première STI (14)

## Régimes sinusoïdaux - circuit RLC série


Circuit RLC Série:  $i(t) = I\sqrt{2} \cos \omega t$   
 $u(t) = U\sqrt{2} \cos(\omega t + \varphi)$



Fresnel

$$\vec{U} = \vec{U}_R + \vec{U}_L + \vec{U}_C$$
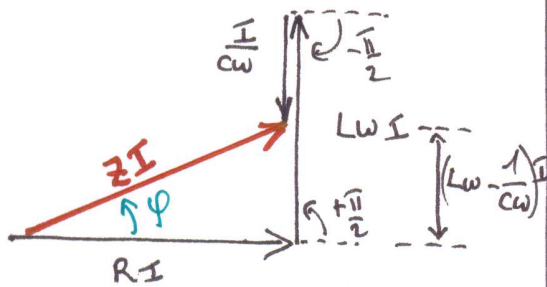
$$\vec{U} \begin{cases} ZI \\ \varphi \end{cases} \quad \vec{U}_R \begin{cases} RI \\ 0 \end{cases} \quad \vec{U}_L \begin{cases} L\omega I \\ +\frac{\pi}{2} \end{cases} \quad \vec{U}_C \begin{cases} \frac{I}{C\omega} \\ -\frac{\pi}{2} \end{cases}$$



$$Z = \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}$$

$$\tan \varphi = \frac{L\omega - \frac{1}{C\omega}}{R}$$

nombres complexes

$$\underline{U} = \underline{U}_R + \underline{U}_L + \underline{U}_C$$

$$\underline{U} = \underline{Z} \underline{I} \quad \underline{U}_R = R \underline{I} \quad \underline{U}_L = jL\omega \underline{I} \quad \underline{U}_C = -j \frac{I}{C\omega}$$

ou  $\underline{Z}_R = R$   $\underline{Z}_L = jL\omega$  et  $\underline{Z}_C = -j \frac{1}{C\omega}$

$$\underline{U} = \underline{Z}_R \underline{I} + \underline{Z}_L \underline{I} + \underline{Z}_C \underline{I}$$

$$\underline{U} = (\underline{Z}_R + \underline{Z}_L + \underline{Z}_C) \underline{I}$$

$$\underline{U} = \underbrace{\left[ R + j \left( L\omega - \frac{1}{C\omega} \right) \right]}_{\text{impédance complexe}} \underline{I}$$

$$\underline{Z} = R + j \left( L\omega - \frac{1}{C\omega} \right)$$

module  $\underline{Z} = Z = \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}$

$\arg \underline{Z} = \tan^{-1} \left( \frac{L\omega - \frac{1}{C\omega}}{R} \right) = \varphi$   
 ↓  
 déphasage de  $u$  %  $i$